



Verilog.

P.C. No.1

Anshuman Singh, OM Thakur
260240133004, 260240133624

Assignment -17



Q Mealy :- 1001

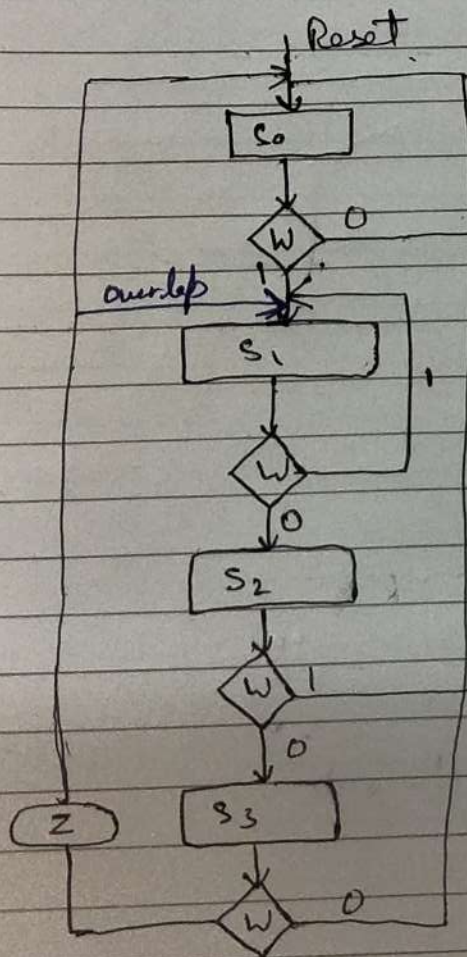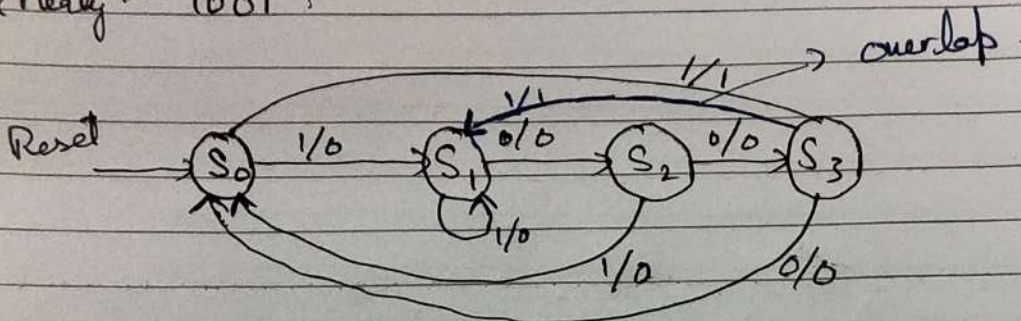


$w \rightarrow$ Input
 $z \rightarrow$ Output

Mealy:

Q2. 10101 -

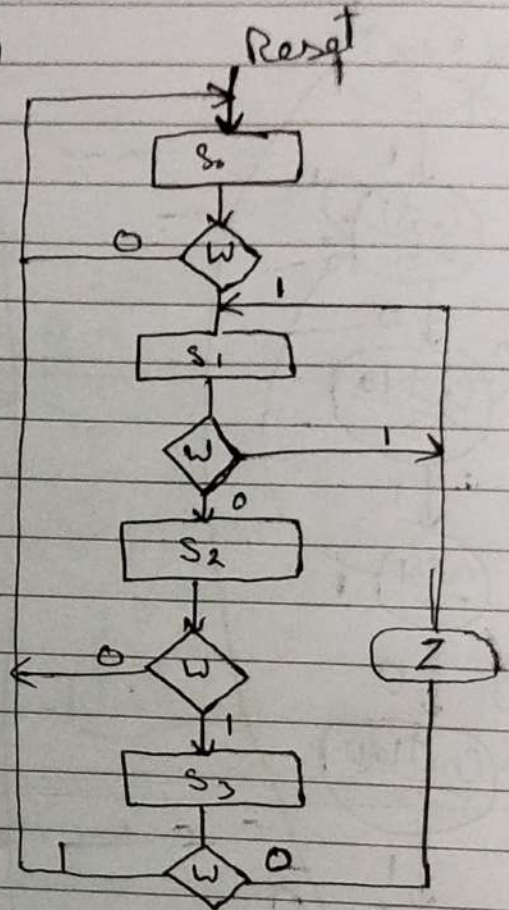
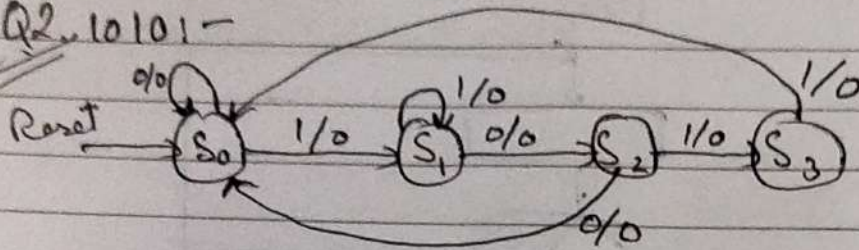


Q3 1011 & 1010 -

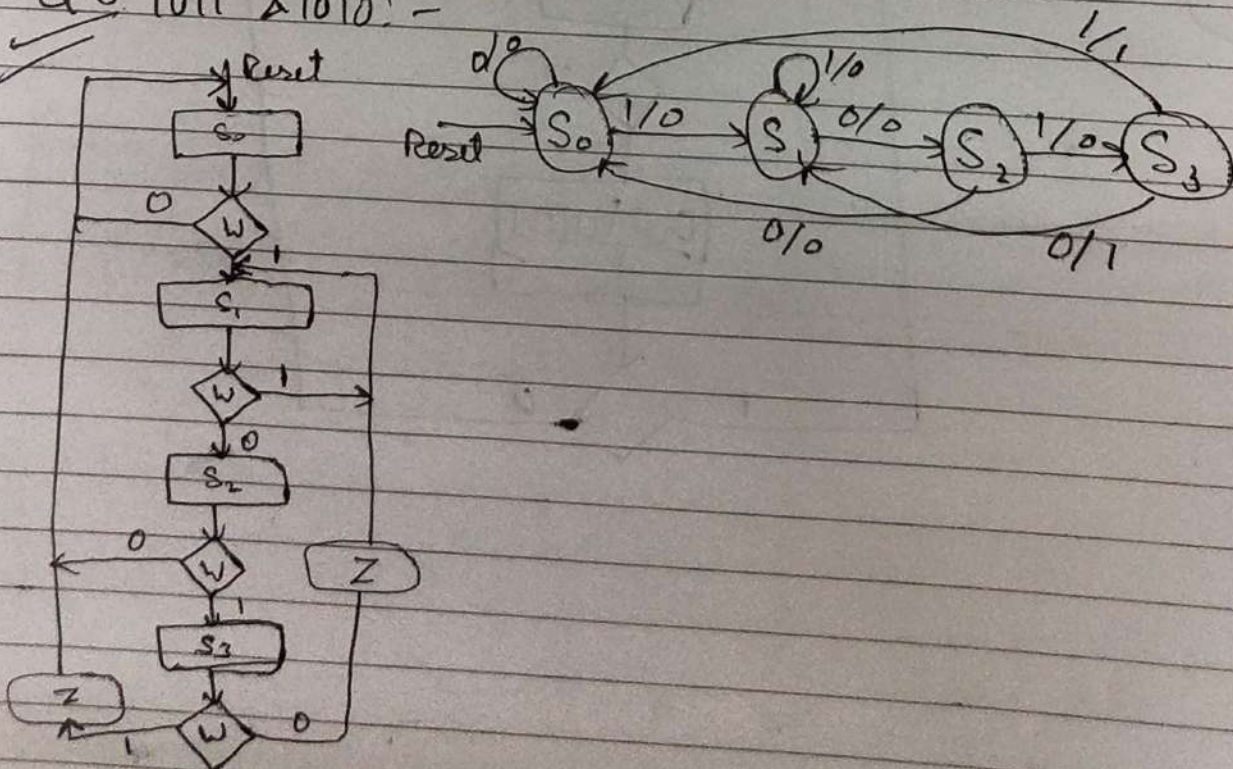

Moore:-

Q1 10101:-

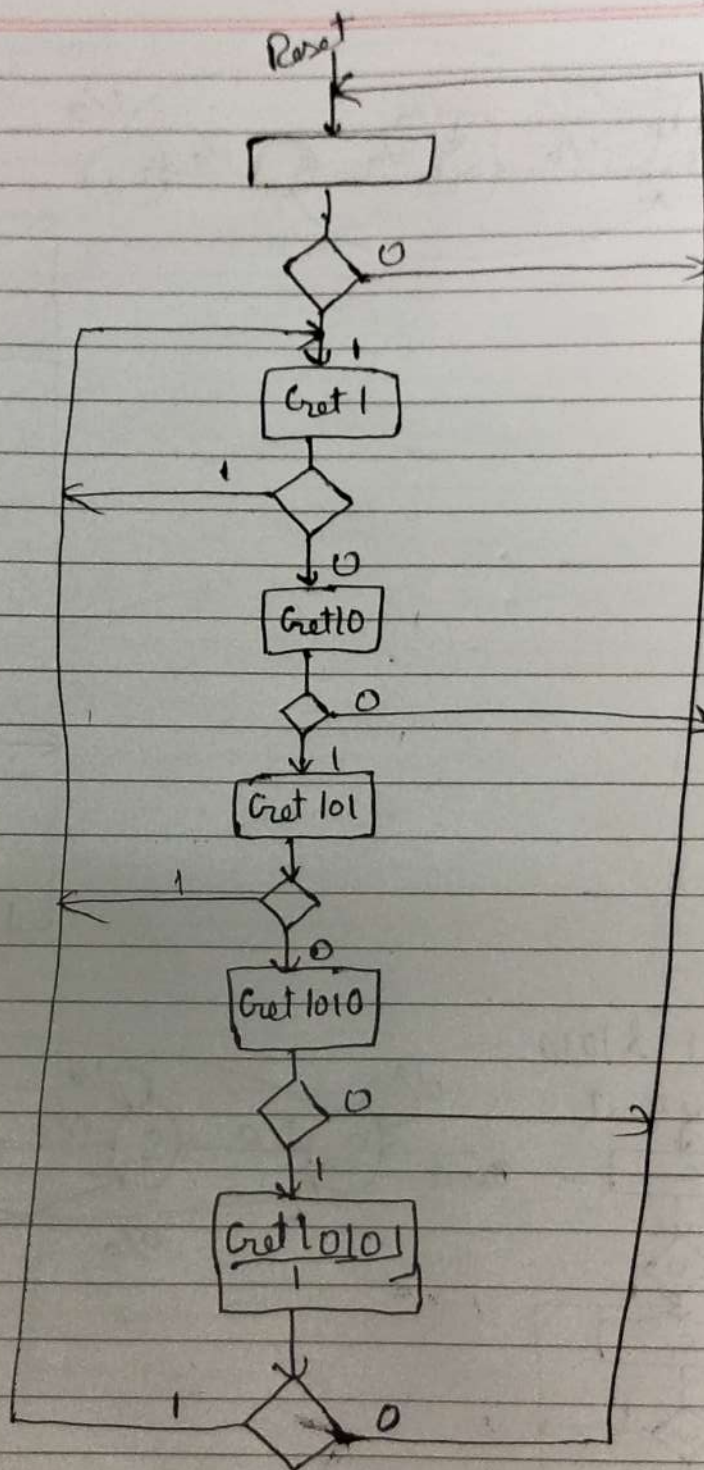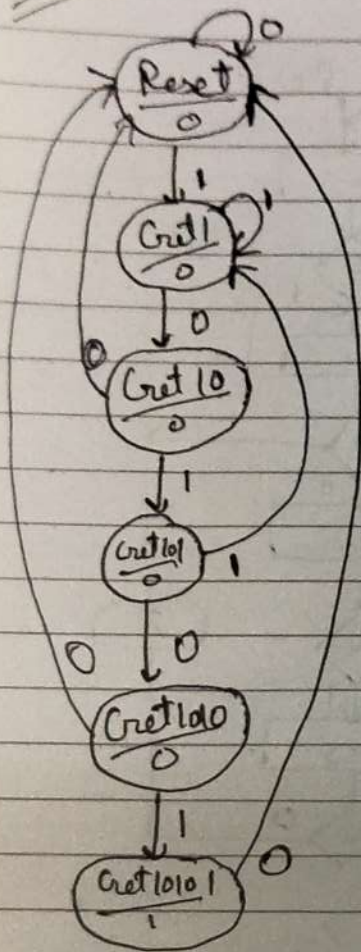

Maare

Q2 10010210101:-

